
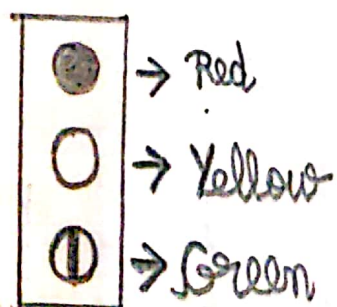


A 4 way junction with traffic signals

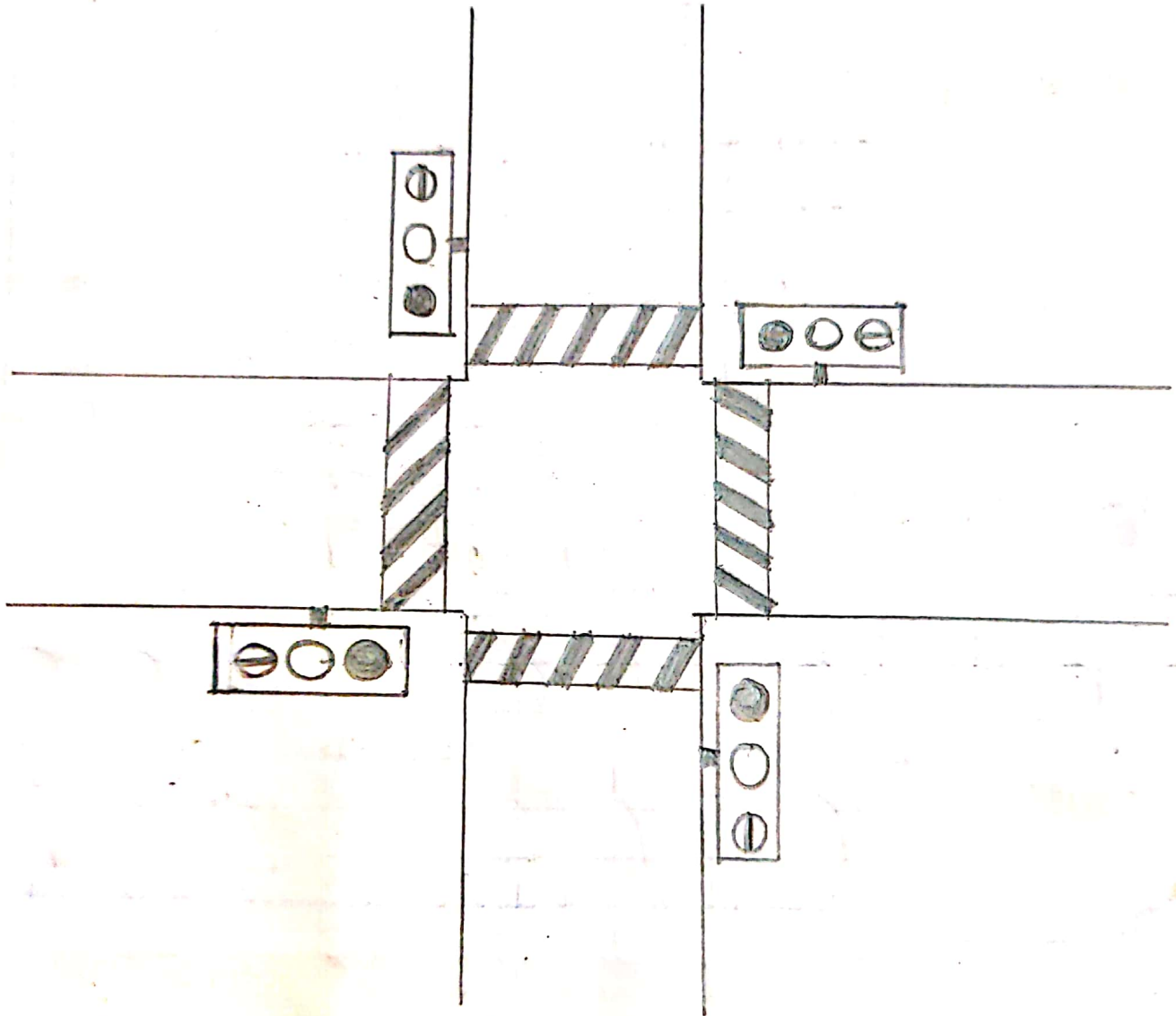

## A Prototype signal of a 4 way junction using a D-flip flop

Aim: To create a working prototype of a 4 way traffic signal using a D flip flop

Apparatus required:

S.No	Component	Specification	Qty
1	D-flipflop	IC 74 74	2
2	NOT gate	IC 74 04	1
3	NAND gate	IC 74 08	1
4	IC Trainer kit	—	1
5	Patch cords	—	30

Procedure:


- Assemble and connect the above components in the IC trainer kit
- Give the connections as per the circuit diagram
- Verify the truth table

Description:


- This project demonstrates the implementation of Shift registers using a D flip flop in a 4 way traffic signal
- The output of the D flip flops are used to generate the green signal and the Red signal is obtained by complementing the output of the D-flip flop
- The yellow signal is generated with the help of the clock pulse and a NAND Gate.



# Pin Diagram

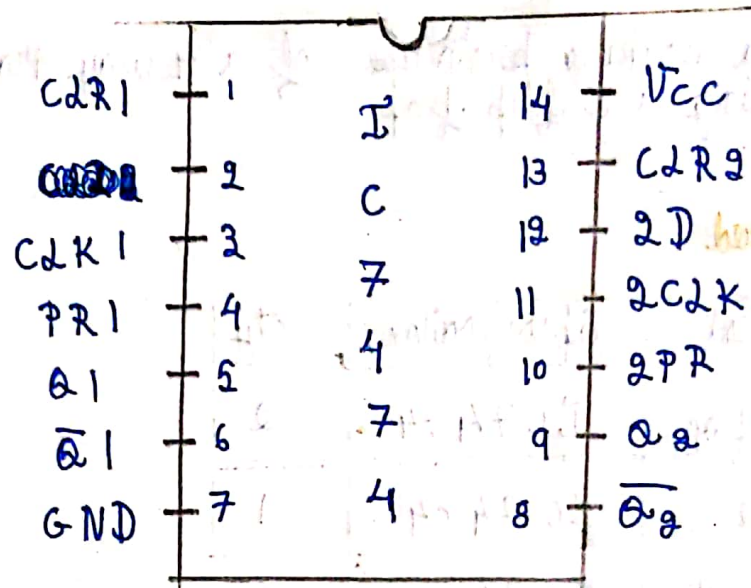

## Circuit Diagram

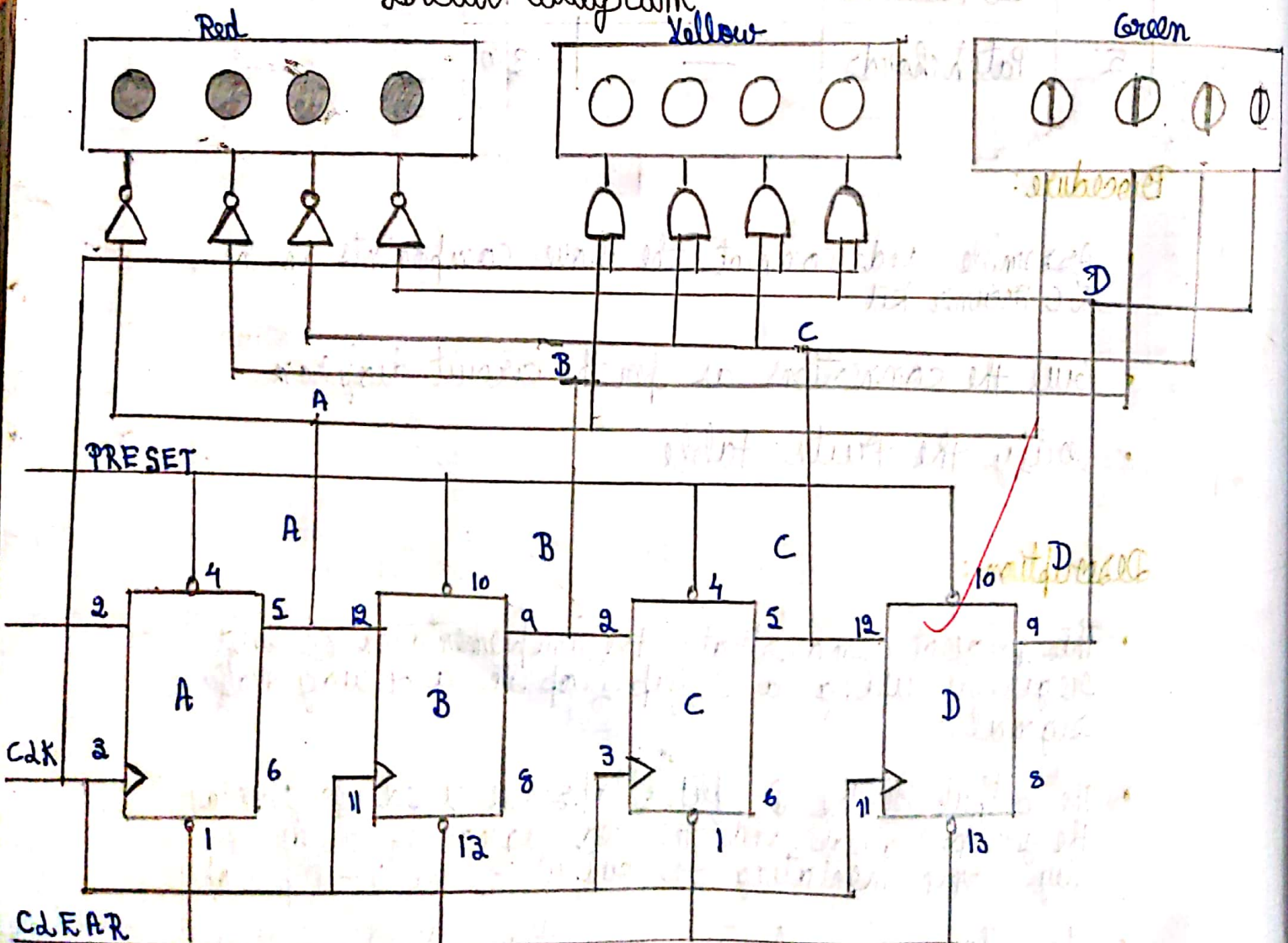



- The logical configuration of shift register consist of D-flip flops cascaded with the output of one flip flop connected to the input of the next flip flop
- All the flip flops receive a common clock pulse which causes the shift in the output of the flip flop, i.e., the traffic signal
- The output of a given flip flop is connected to the input of the next flip flop of the register

Truth table

clk	Data	output							
		Red				Green			
		A	B	C	D	A	B	C	D
1	1	0	1	1	1	1	0	0	0
2	0	1	0	1	1	0	1	0	0
3	0	1	1	0	1	0	0	1	0
4	0	1	1	1	0	0	0	0	1
5	0	1	1	1	1	0	0	0	0

When CLK

Explanation

- 1  $\longrightarrow$  A is Green & B, C, D are Red
- 2  $\longrightarrow$  B is Green & A, C, D are Red
- 3  $\longrightarrow$  C is Green & B, C, D are Red
- 4  $\longrightarrow$  D is Green & A, C, B are Red
- 5  $\longrightarrow$  All the lights are red for the pedestrians to cross